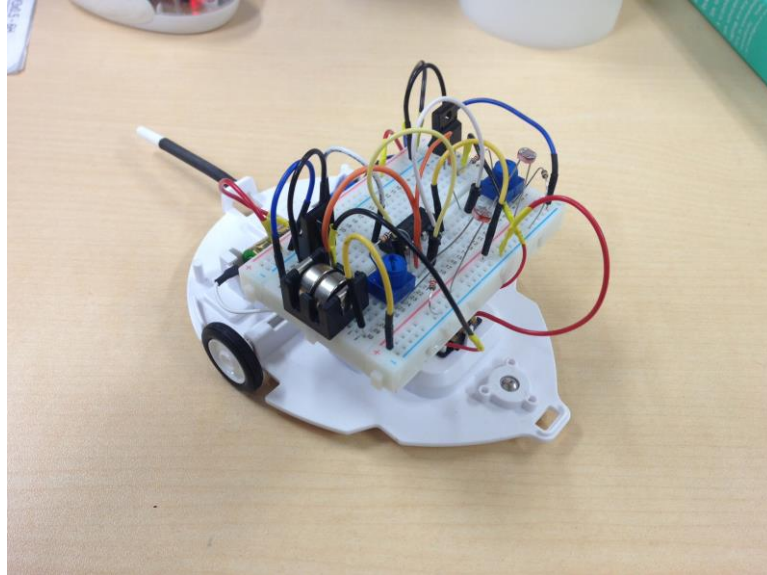


## Light Following Mouse Robot (by Joshua Supratman)

Purpose of this tutorial is to create a simple robot with adjustable circuit to create different effects



### Materials

- N-ch FET K2232 x2



- Resistor 1k $\Omega$  x 4




- Variable Resistor 10 k $\Omega$  x2



- Cds cell 5mm 0.5M $\Omega$  x2



- Bread board

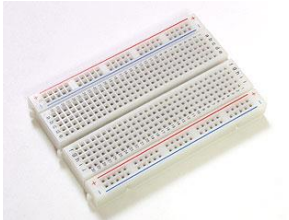

- Coin battery LR44 x2



- Coin battery holder MPD BH1/3N-C CR1 3N 用(LR44 2 個)電池ボックス




- Insulator tape




- Wire Stripper



- Nipper

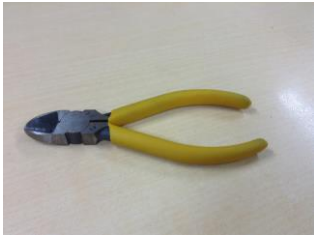


- Wires

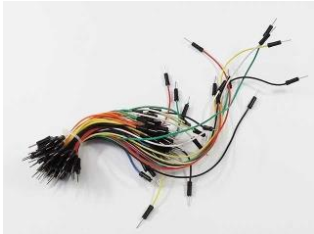

- Tamiya's Mouse Robot




- (optional) Inverter IC

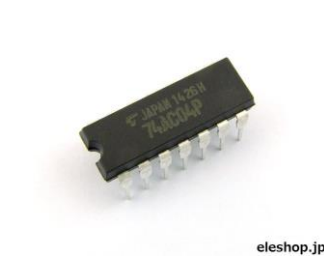


elishop.jp

- (optional) AND logic IC

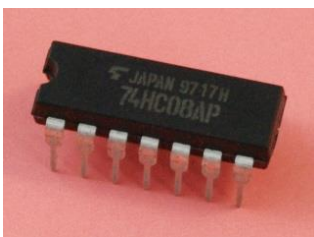


- (optional) flash light


How to make jumper wire

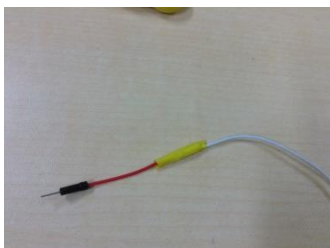

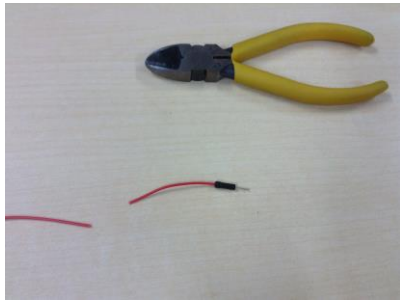
- 1) Use the nipper to cut the desired wire and the jumper wire



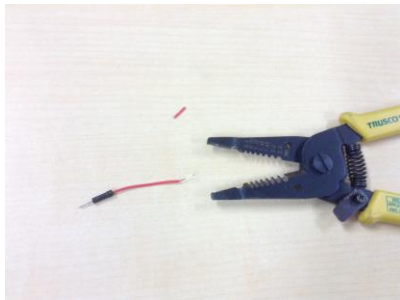
- 2) Use the wire stripper to strip at least 1 cm of wire



- 3) Make small hooks as shown below

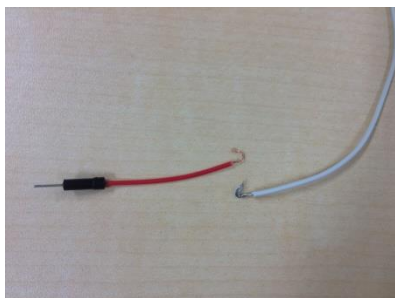


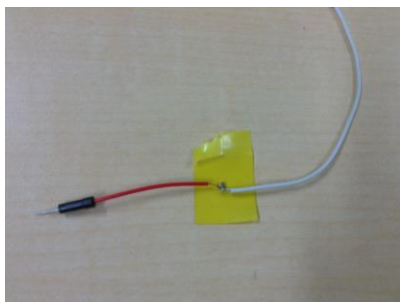- 4) Bind the wires together and cover it using vinyl tape




How to make

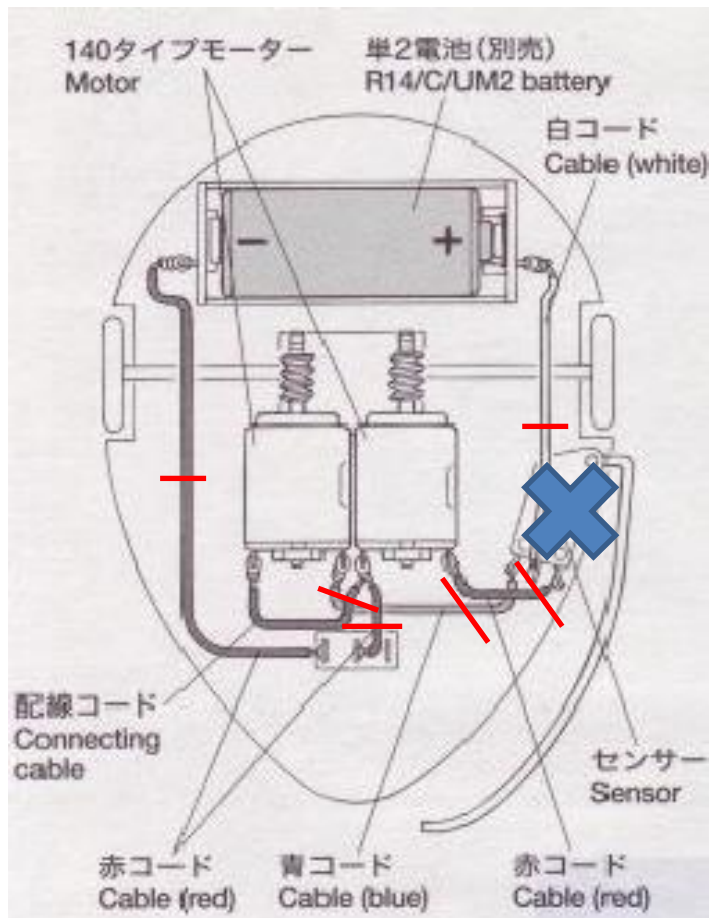- 1) Follow the Tamiya's Mouse Robot instruction and make the robot
- 2) Remove the switch and cut the unnecessary wires



- 3) Make jumper wires of the motor and the battery (refer to /jumperwires)
- 4) Place the motor's jumper wires over the gearbox and toward the battery
- 5) Place the bread board on top of the gearbox
- 6) Design the circuit

Circuit:

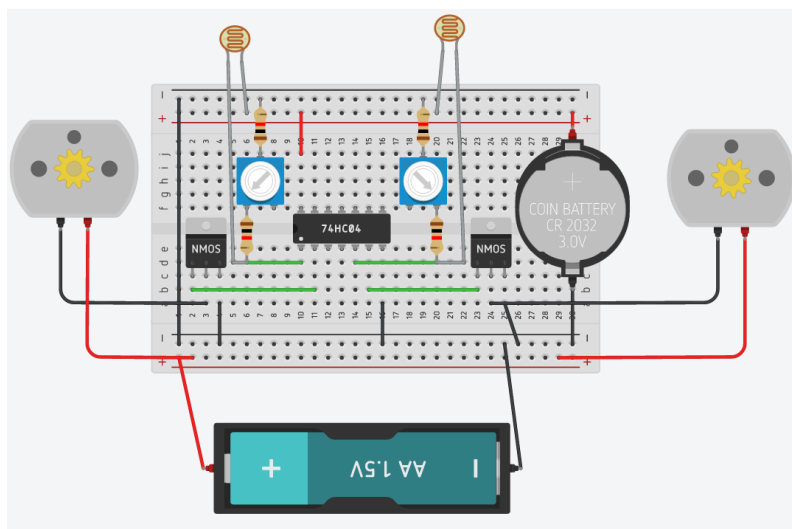


How to use


- 1) Rotate the variable resistor until the motor stop moving
- 2) Rotate the variable resistor and find the value just before the motor start moving
- 3) Use external light source or your hand and cover the cds cell to control the robot
- 4) Redesign circuit for your own use (refer to /circuit)

Circuit Variation:


Pull Up Resistor

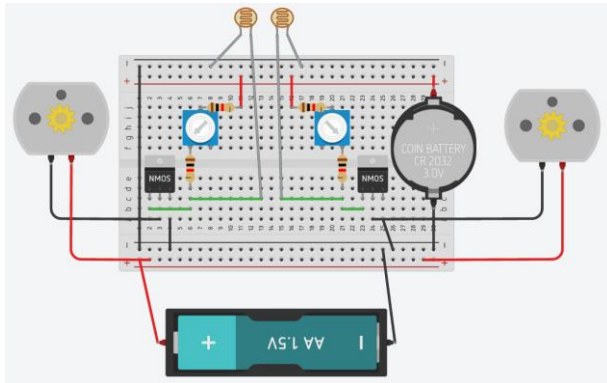


Pull Down Resistor

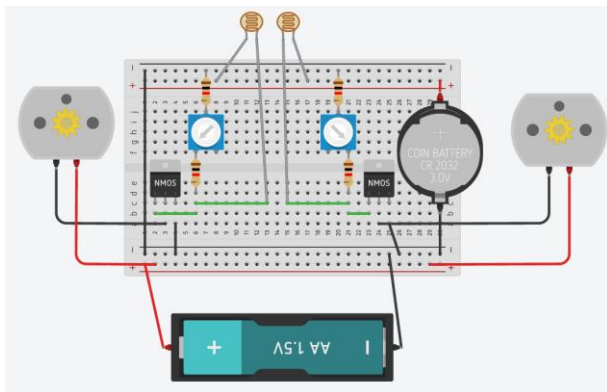


AND with Pull Up Resistor

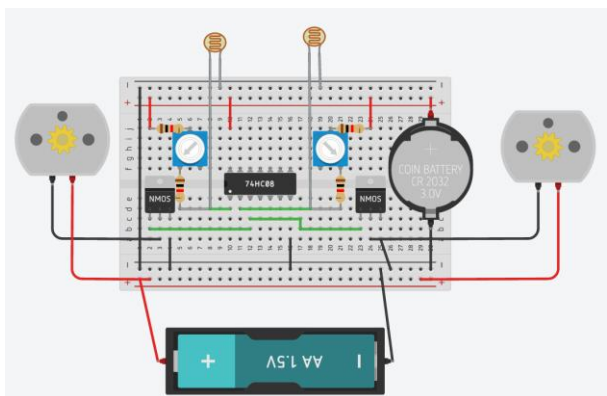


AND with Pull Down Resistor

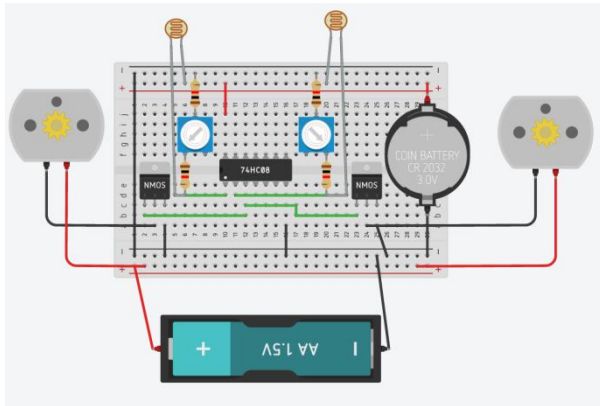

NOT with Pull Up Resistor

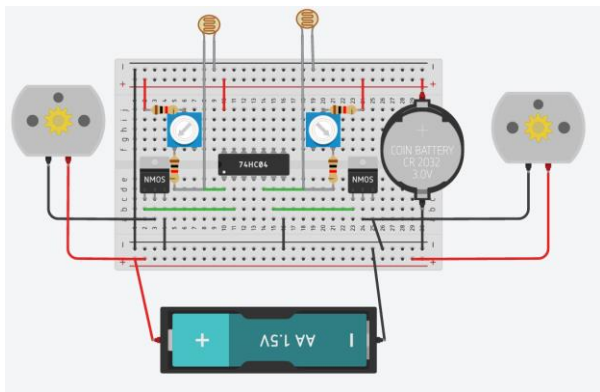

NOT with Pull Down Resistor

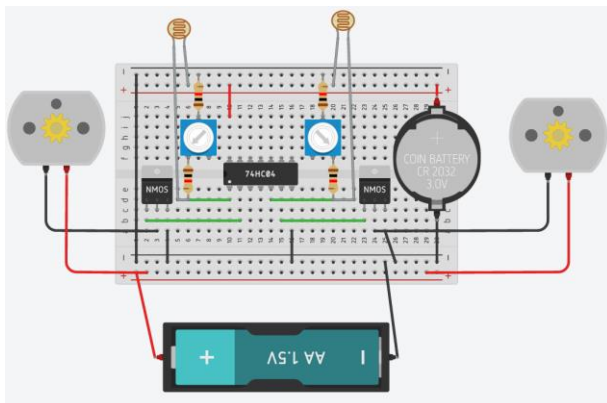

Extra:

Different circuit can be used to create different effect. Can you make a circuit that can do one of the following?

- 1) Follow the light?
- 2) Follow the shadow?
- 3) Run from light?
- 4) Wander to find light?

5) Stop when spotted?

How will the robot move when you make the following circuit?

- 1) Mixture of AND and NOT logic IC
- 2) Using different logic IC